

Assignment 11

UTTAKARSHIKA
CS20B1023
IIIT RAICHUR

6TH JANUARY, 2021

1 Problem

- EC GATE 2015, 37


2 Solution

- Propagation Delay
- Timing Diagrams
- Truth Table
- Conclusion

 Problem Statement

EC GATE 2015, 37-


All the logic gates shown in the figure have a propagation delay of 20ns. Let $A=C=0$ and $B=1$ until time $t=0$. At $t=0$, all the inputs flip (i.e., $A=C=1$ and $B=0$) and remain in that state. For $t > 0$, output $Z=1$ for a duration of-



Propagation Delay

Propagation delay refers to the time taken by a signal to reach its destination.

Solution / Timing Diagrams

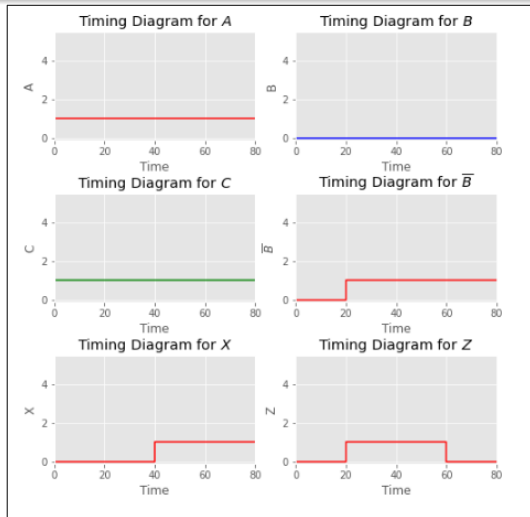

Solution / Truth Table

time(t)	A	B	C	B'	X	Z
<0	0	1	0	0	0	0
0	1	0	1	0	0	0
20	1	0	1	1	0	1
40	1	0	1	1	1	1
60	1	0	1	1	1	0
80	1	0	1	1	1	0

Conclusion

According to the given timing diagram, $Z=1$ for a duration of 20-60ns.

